

CS303 - Logic and System Design

Laboratory Assignment #3

Deadline: 4.12.2022 23.55

In Lab #3, a signed comparator will be designed using Verilog HDL and implemented on FPGA board.

1. Pre-lab Assignment

Design a comparator circuit that takes two 4-bit signed 2's complement binary numbers, A and B, and turns ON one of the three LEDs by comparing them.

Possible three scenarios for the comparator output are $A > B$, $A < B$ and $A = B$. Only one of these three scenarios will be true for any input combinations and only one of the three LEDs will turn ON.

After designing the circuit using Verilog HDL and verifying your design through simulations, the design should be mapped to FPGA. A constraint file is required indicating which switches and LEDs you will use from the FPGA resources. Please note that your design will be implemented during the lab session. However, it is required to prepare the file and upload it to SuCourse as part of the prelab assignment.

For the constraint file, 8 switches and 3 LEDs will be needed. Please use the following switches and LEDs in your constraint file.

Switches for the first 4-Bit Number:

- R15, M13, L16, J15

Switches for the second 4-Bit Number:

- T8, R13, U18, T18

LED for $A > B$: H17

LED for $A < B$: K15

LED for $A = B$: J13

3 files will be submitted for prelab assignment:

1. Project folder of your design including your Verilog codes, simulation files.
2. Constraint file for FPGA implementation.
3. A report explaining all your work in detail.

2. In-Lab Assignment

In the lab you will show your simulation results and implement your designs on the FPGA board.