

## Homework #2

**Q1)**

Do the following conversions.

Decimal	Binary	Hexadecimal
546		
128		
27.375		

Decimal	Signed 8-bit binary in 2's complement form
-6.375	

Signed 8-bit binary in 2's complement form	Decimal
00000011.1101	
11111111.1111	
10100110.0111	

**Q2)**

Calculate the binary equivalent of  $127/64$ . If we use only 4 bits in the fraction, what is the error in the binary representation? How many bits are needed to fully represent  $127/64$  in signed 2's complement binary number system? Show your work clearly.

**Q3)**

Perform the following binary arithmetic operations on two 8-bit signed binary numbers in 2's-complement format and indicate whether there is an overflow or not. Show the intermediate steps.

$$\begin{array}{r} 00111001 \\ + 00111001 \\ \hline \end{array}$$

$$\begin{array}{r} 11111111 \\ + 00000001 \\ \hline \end{array}$$

$$\begin{array}{r} 00111001 \\ - 00111001 \\ \hline \end{array}$$

$$\begin{array}{r} 00000000 \\ - 11111111 \\ \hline \end{array}$$

**Q4)**

Implement  $F = xy + x'y' + y'z$  using only NAND gates.

**Q5)**

$$F(x,y,z,t) = (x \oplus y)(z+t)$$

- Express the following function as a sum of minterms.
- Express the following function as a product of maxterms.
- Optimize F using Karnaugh map.

- d) Assume we guarantee that  $xyzt$  will never be larger than 12. Add necessary don't care conditions and optimize  $F$  further using K-map.

### Q6)

Design a combinational circuit that divides a 2-bit unsigned binary number  $A = (a_1 a_0)$  by another 2-bit unsigned binary number  $B = (b_1 b_0)$  and generates a 2-bit unsigned binary number  $D = (d_1 d_0)$  that gives the remainder of the division (i.e.  $D = A \% B$ ). Note that division-by-0 is not defined. Therefore, you can assume that the input combinations causing division-by-0 are not applied.

$a_1$	$a_0$	$b_1$	$b_0$	$d_1$	$d_0$
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

- a) Derive the truth table.
- b) Derive simplified boolean expressions for the outputs in sum-of-products form using K-maps.
- c) Implement d0 output using NOR gates only and draw the circuit.

**Q7)**

Design a magnitude comparator that takes two 3-bit signed numbers in 2's complement format,  $A = (a_2 a_1 a_0)$  and  $B = (b_2 b_1 b_0)$ , and outputs  $g = 1$  if  $A > B$ , otherwise  $g = 0$ . Show the boolean expression for the output  $g$